

Electric Circuits 2

Lab: 02

Jaden Moore

Orange Coast College
Physics A285L
December 7th, 2021

1 Introduction

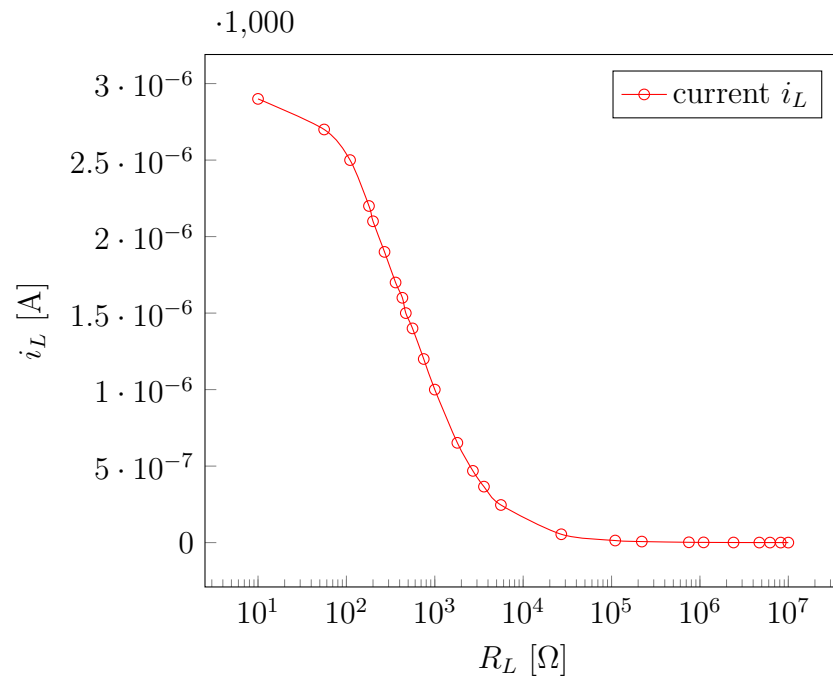


Figure 1: Voltage through load resistance R_L

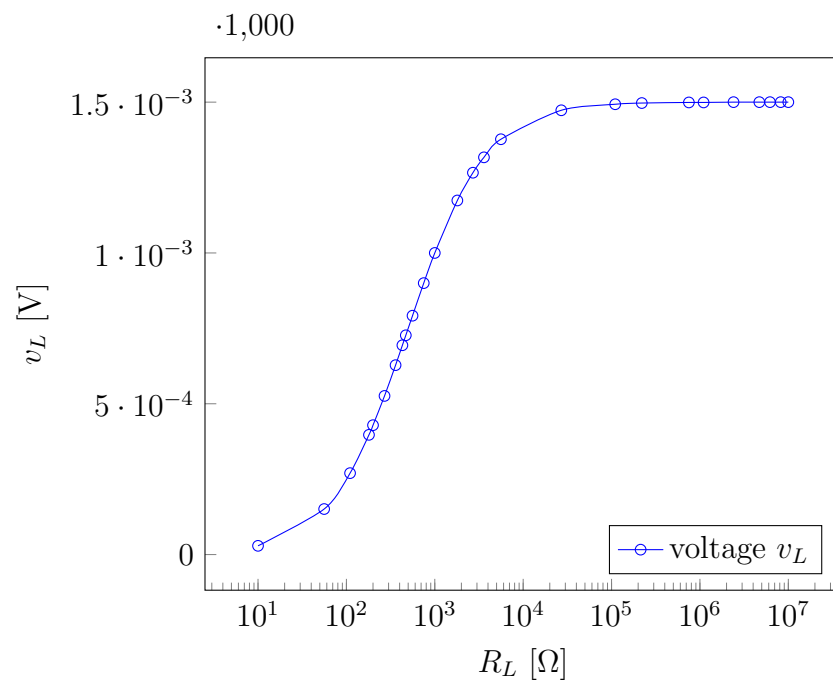


Figure 2: Current through load resistance R_L

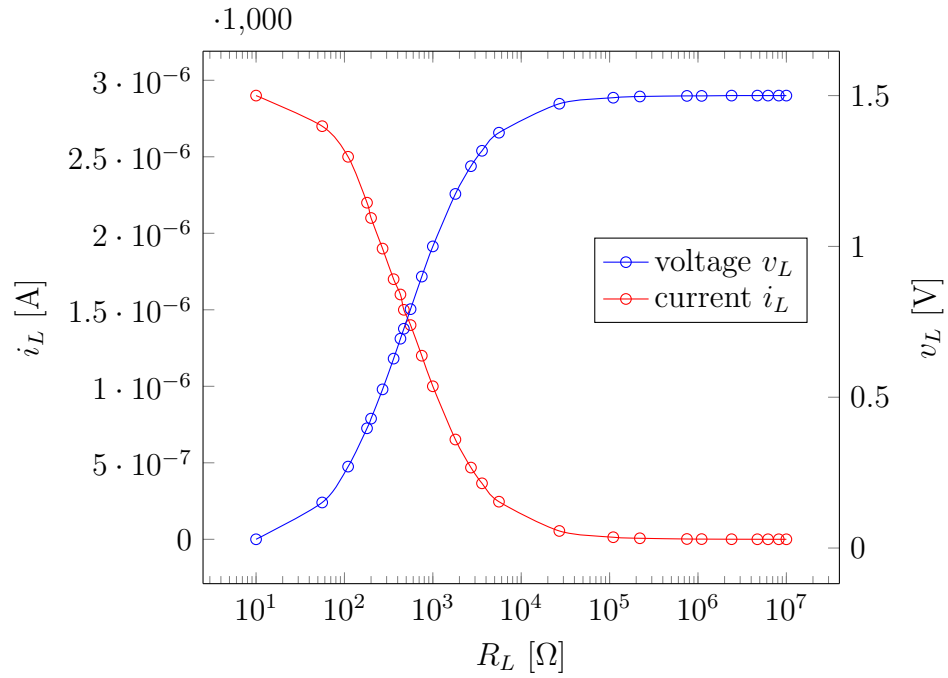


Figure 3: Current and voltage through load resistance R_L

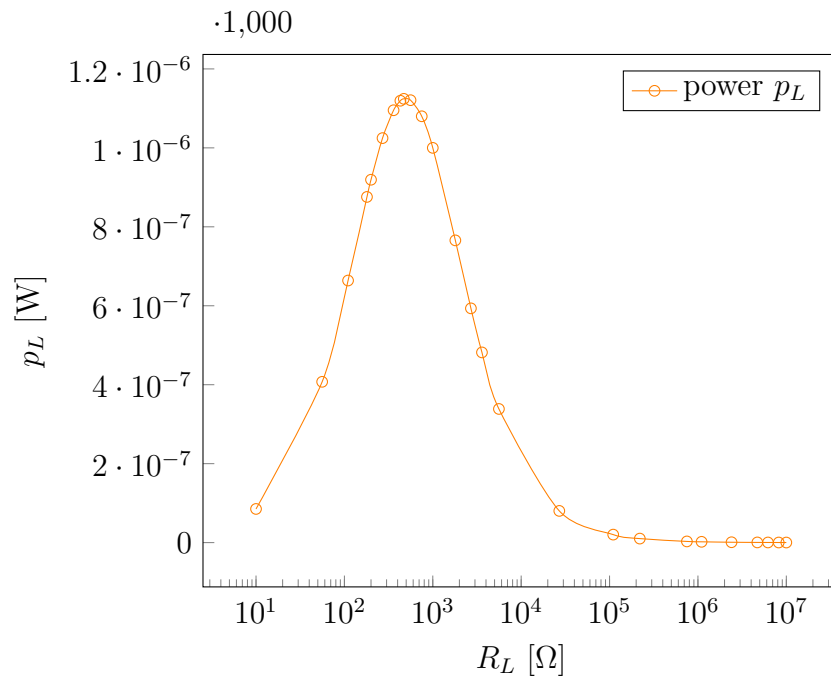


Figure 4: Power p_L through load resistance R_L