

Electric Circuits 2

Lab: 02

Jaden Moore

Orange Coast College
Physics A285L
December 7th, 2021

1 Introduction

In this lab, we attach a resistance R_L across two end terminals of a circuit. We then analyze the behavior of the various electrical quantities across the resistor as resistance increases. We then prove Thévenin's theorem by creating Thévenin's equivalent circuit and comparing the electrical quantities with the original circuit quantities.

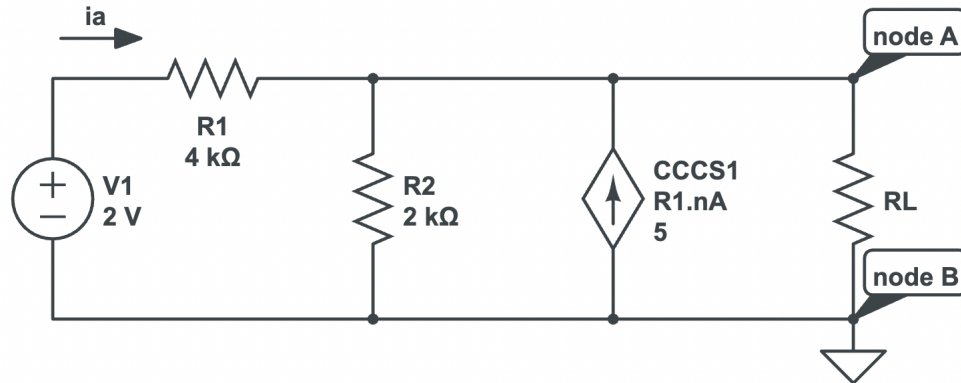


Figure 1: Electric circuit with resistor R_L across terminals A-B

Consider the circuit presented in Figure (1). We place increasing resistances across R_L and measure the current i_L , the voltage, v_L , and power p_L across the resistor and record the data in the table below.

Table 1: Recorded image and object distances from the lens

| R_L [Ω] | i_L [A] | v_L [V] | p_{L-exp} [W] | $p_{L-theory}$ [W] |
|--------------------|--------------|--------------|-----------------|--------------------|
| 10 | 294.1E-05 | 0.029 | 086.5E-06 | 269.8E-05 |
| | | | 086.5052E-06 56 | |
| 0.151 | 407.6E-06 | 245.9E-05 | 0.27 | 001.025E-03 |
| | 407.5876E-06 | | | 001.0246E-03 |
| | 110 | | | 180 |
| 220.6E-05 | 0.397 | 875.9E-06 | 214.3E-05 | 0.429 |
| | | 875.8651E-06 | | |
| | | 200 | | |
| 918.4E-06 | 194.8E-05 | 0.526 | 001.0E-03 | 174.4E-05 |
| 918.3673E-06 | | | 001.0246E-03 | |
| 270 | | | 360 | |
| 0.628 | 001.1E-03 | 161.3E-05 | 0.694 | 001.1E-03 |
| | 001.0952E-03 | | | 001.1186E-03 |
| | 430 | | | 470 |
| 154.6E-05 | 0.727 | 112.4227E-05 | 112.3924E-05 | |
| 560 | 141.5E-05 | 0.792 | 112.0755E-05 | 112.1396E-05 |
| 750 | 120.0E-05 | 0.9 | 108.0000E-05 | 108.0000E-05 |
| 1000 | 100.0E-05 | 1 | 100.0000E-05 | 100.0000E-05 |
| 1800 | 652.2E-06 | 1.174 | 765.6522E-06 | 765.5955E-06 |
| 2700 | 468.8E-06 | 1.266 | 593.4375E-06 | 593.2617E-06 |
| 3600 | 365.9E-06 | 1.317 | 481.8293E-06 | 481.8560E-06 |
| 5600 | 245.9E-06 | 1.377 | 338.6066E-06 | 338.6187E-06 |
| 27000 | 545.5E-07 | 1.473 | 803.4545E-07 | 803.3058E-07 |
| 110000 | 135.7E-07 | 1.493 | 202.6697E-07 | 202.6986E-07 |
| 220000 | 680.3E-08 | 1.497 | 101.8367E-07 | 101.8094E-07 |
| 750000 | 199.9E-08 | 1.499 | 299.6003E-08 | 299.6004E-08 |
| 1100000 | 136.3E-08 | 1.499 | 204.3162E-08 | 204.3596E-08 |
| 2400000 | 624.9E-09 | 1.5 | 937.3047E-09 | 937.1095E-09 |
| 4700000 | 319.1E-09 | 1.5 | 478.6725E-09 | 478.6216E-09 |
| 6200000 | 241.9E-09 | 1.5 | 362.8740E-09 | 362.8447E-09 |
| 8200000 | 182.9E-09 | 1.5 | 274.3735E-09 | 274.3568E-09 |
| 10000000 | 150.0E-09 | 1.5 | 224.9888E-09 | 224.9775E-09 |

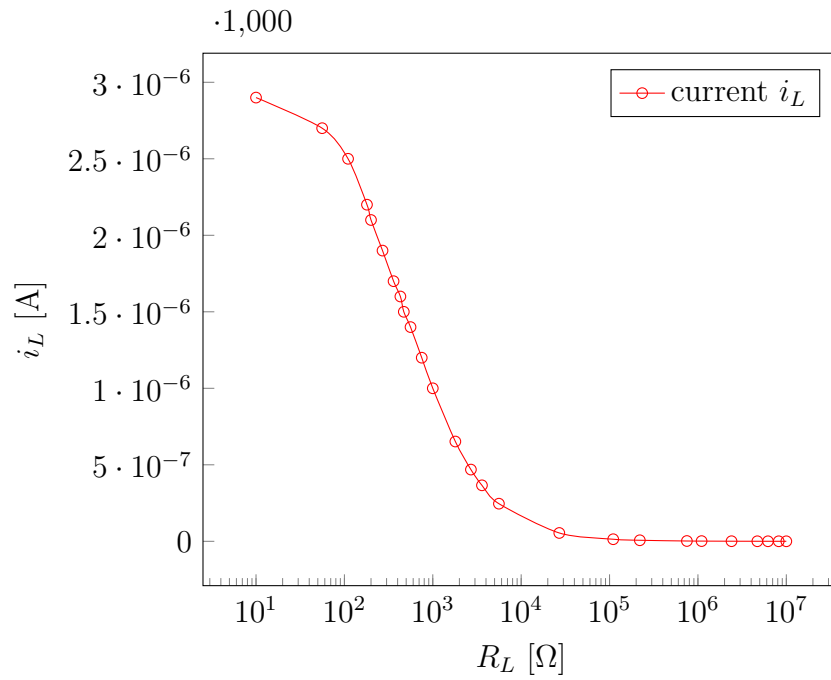


Figure 2: Current through load resistance R_L

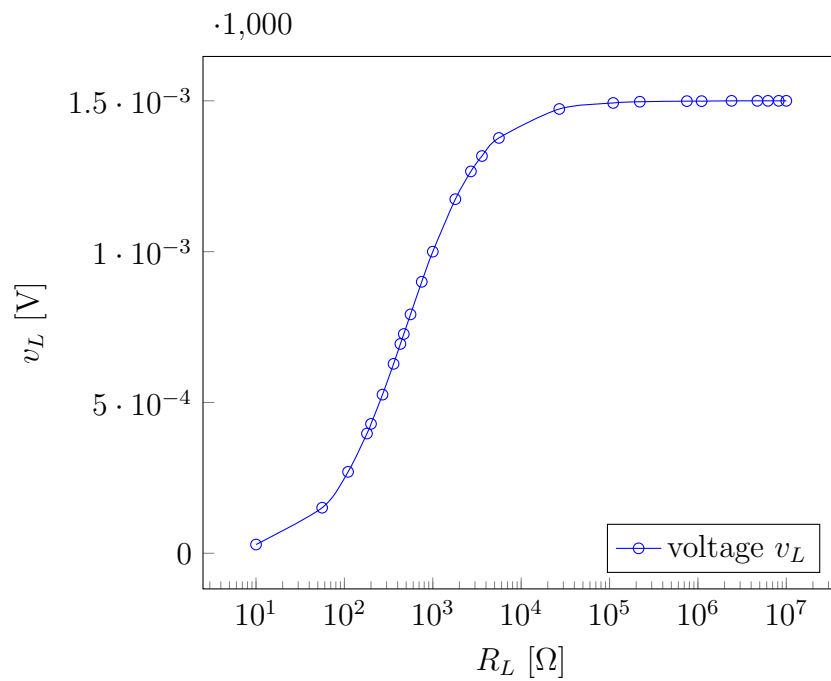


Figure 3: Voltage through load resistance R_L

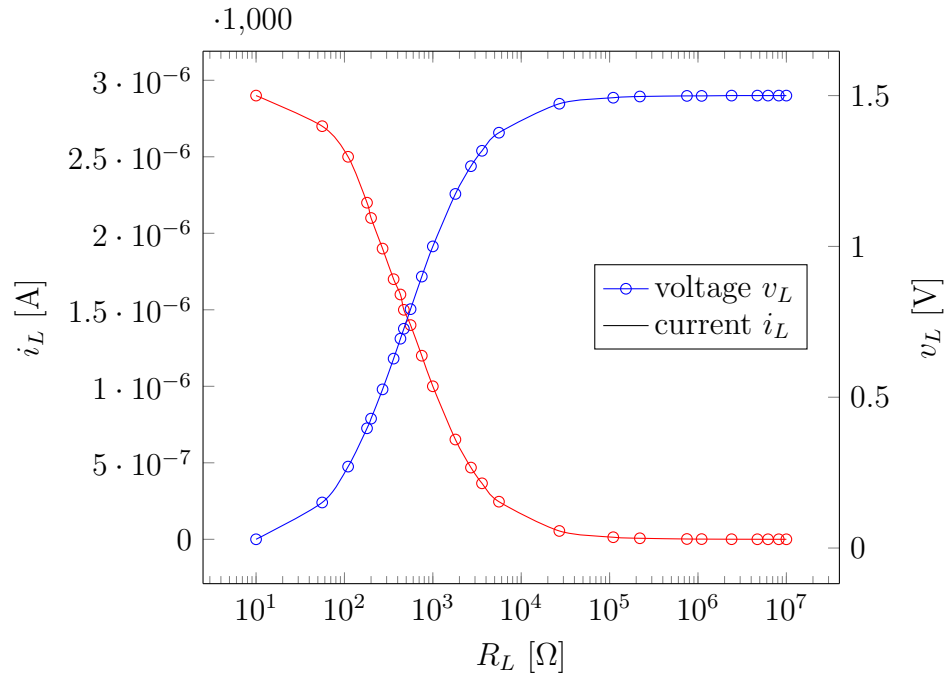


Figure 4: Current and voltage through load resistance R_L

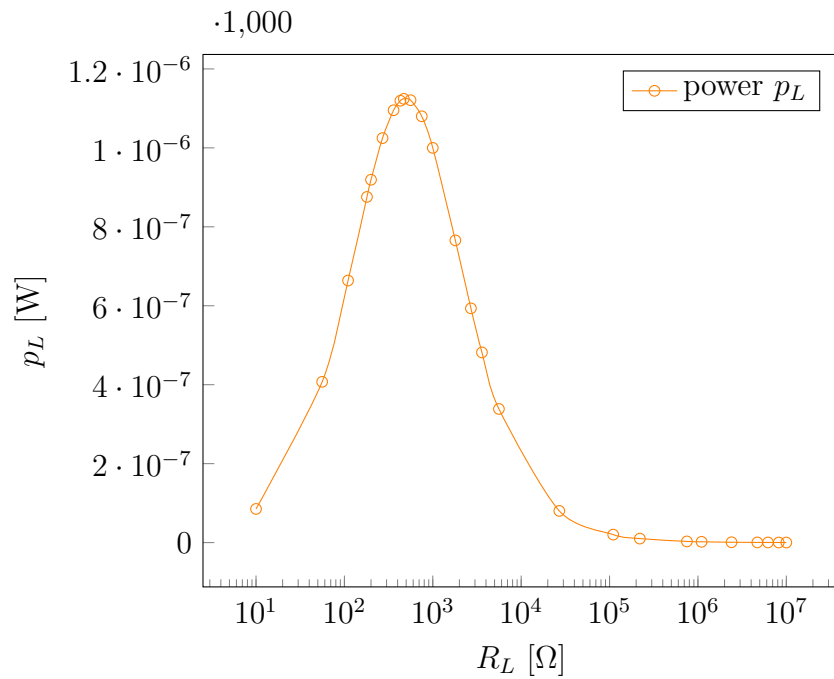


Figure 5: Power p_L through load resistance R_L