

Circuit Analysis

Lab: 05

Jaden Moore

Orange Coast College
Physics A280L
April 13th, 2021

1 Introduction

In this lab, we analyze the properties of an electric circuit to find the resistance of each bulb on the circuit. Consider the circuit provided by Physlet® Physics - Exploration 30.2: Lightbulbs. Below we analyze the properties of the circuit and determine the resistance of the lightbulbs at each point.

2 Circuit Analysis

(a) We can see that when one switch is open and the other is closed, bulb C becomes in series with one of the bulbs depending on which switch was closed. The current becomes larger to the bulb because when one switch is opened, it is no longer in parallel with the other bulb so the total resistance to the current gets smaller, thus the bulb gets brighter.

(b) We can see that when switch S_1 is closed and switch S_2 is open, the current through the circuit is 1.00 A.

(c) When switch S_1 is closed and switch S_2 is open, the current through the circuit is still 1.00 A.

(d) This proves that bulb R_A and bulb R_B are identical because from Ohm's law, we have $R = \frac{\Delta V}{I}$ and since the voltage is the same across both bulbs R_A and R_B because they are connected in parallel and, the current is the same between both of them because they have the same brightness, thus $R_A = R_B$

(e) When one switch is open and one is closed, the brightness of bulb R_C is equivalent to the bulb it is in series with.

(f) This indicates that the resistance of bulb R_C is also equal to the resistance of bulb R_A and R_B

(g)

i. The combined resistance of R_A and R_B since they are connected in parallel can be calculated as such:

$$\begin{aligned}\frac{1}{R} &= \frac{1}{R_A} + \frac{1}{R_B} \\ \frac{1}{R} &= \frac{1}{R_A} + \frac{1}{R_A} \\ \frac{1}{R} &= \frac{2}{R_A} \\ R &= \frac{1}{2}R_A\end{aligned}$$

ii. Since R_C is in series with the parallel resistors R_A and R_B when both switches are closed, we can use the fact that the bulbs are series in to get the effective resistance of the circuit, thus:

$$R_{eq} = \frac{1}{2}R_A + R_C$$

(h) When both switches are closed, we get the effective resistance R_1 from Ohm's law to be:

$$R_1 = \frac{\Delta V}{I} = \frac{20}{\frac{4}{3}} = 15 \Omega$$

Thus, we get that:

$$\begin{aligned} \frac{1}{2}R_A + R_C &= R_1 \\ \frac{1}{2}R_A + R_C &= 15 \Omega \end{aligned}$$

(i) When one switch is closed, Bulb R_C is in series with either R_A or R_B . Thus, if we take it when S_2 is closed, we get R_2 :

From Ohm's Law:

$$R_2 = \frac{\Delta V}{I} = \frac{20}{1} = 20 \Omega$$

Thus, since R_C is in series with R_A , we get that:

$$\begin{aligned} R_A + R_C &= R_2 \\ R_A + R_C &= 20 \Omega \end{aligned}$$

(j) Setting up the equations obtained in (h), we get the following setup:

$$\begin{aligned} R_A + R_C &= 20 \Omega \\ \frac{1}{2}R_A + R_C &= 15 \Omega \end{aligned}$$

Solving the series of equations, we get:

$$R_A = 20 - R_C$$

$$\frac{1}{2}(20 - R_C) + R_C = 15 \Omega$$

$$10 - \frac{1}{2}R_C + R_C = 15 \Omega$$

$$R_C = 10 \Omega$$

$$R_A + R_C = 20 \Omega$$

$$R_A + 10 = 20 \Omega$$

$$R_A = 10 \Omega$$

Thus,

$$R_A = R_B = 10 \Omega$$

$$R_C = 10 \Omega$$

3 Conclusion

From the lab, we get that the resistance across all three bulbs is equivalent to each other at 10Ω . We predicted this in the beginning based on the brightness of the bulbs after opening and closing the switches. The greatest obstacle was viewing the circuit differently in a way that makes it quicker to solve. Before this, One would use Kirchhoff's loop laws to solve the circuit which would take much more time to solve. The biggest takeaway is understanding how to analyze circuits in different ways to same time and be more efficient in solving problems.